

P2: Electricity and magnetism **Knowledge organiser**

Resistance

The resistance is a measure of how easy it is to pass through a component.

conductors - low resistance

insulators - high resistance

Resistance is calculated by measuring the potential difference and the current.


The unit for resistance is the **ohm** (Ω).

Magnets

- Magnets have north and
- · Opposite poles attract, and the same

Magnetic fields

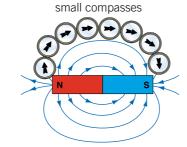
- A magnet has a field around it.
- You can see the field around a bar magnet with a small compass or iron filings.
- If the lines are close together the field is stronger.



• The Earth has a magnetic field, which acts like a big bar magnet, with the south pole at the top of the planet.

Circuits and currents

- south poles.
- poles repel:

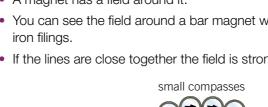

Applying a current to a coil of wire makes it electromagnetic.

turned off.

using more current.


making motors and speakers

How motors work

 Current is the amount of charge flowing per second. • It is measured with an ammeter (connected in series). The unit for current is the amp (A). Key terms Make sure you can write definitions for these key terms. electric field electromagnet insulator magnetic field line ammeter attract conductor current electron repel magnet motor north resistance series static electricity south pole volt voltmeter

Charging up

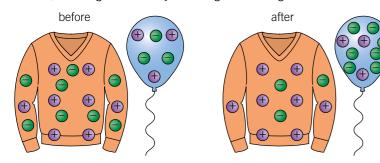Static electricity: by rubbing insulators together electrons are transferred, which gives the objects magnetic charges.




Like charges **repel**, and opposite charges **attract**. Charged objects have **electric fields** around them. These lines show how a positive charge will act.

Series and parallel circuits

In a series circuit all of the components are connected in one loop. If one component or wire breaks, current stops flowing everywhere.


Series circuits

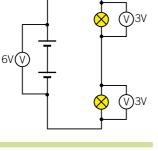- contain only one loop
- the current is the same everywhere
- the **potential difference** across each component adds up to the potential difference across the battery



Parallel circuits

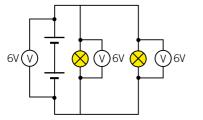- contain multiple branches
- currents in all the branches add up to make the total current
- the potential difference across each component is the same as the potential difference across the battery








Electromagnets

• Electromagnets are only magnetic when they have a flow of current, so they can be

They are made by running a current through a coil of wire.

• They usually have an iron core in the middle of the coil, which makes them stronger.

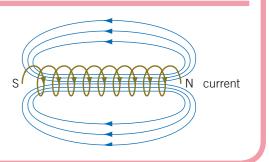You can make an electromagnet stronger by: · adding more turns of wire on the coil



Uses of electromagnets

• moving cars or other metal objects • sorting iron and steel from aluminium

· making levitating trains, which travel much faster as there is no friction

This causes a force between the coil of wire and the permanent magnet nearby, driving a motor.

Potential difference

• Potential difference is the amount of energy transferred by the charges in the circuit. • It is measured with a voltmeter (connected in parallel). The unit is the volt (V).

•••	••••		• • • • • • • • • • • • • • • • • • • •	n,
oole	ohm	parallel	potential difference	